

Resistors classification

Resistors

$\beta_c$


	$R_s [\square \Omega]$	$\Delta R/R [\%]$	$k_T [ppm/^\circ C]$	$\frac{ppm}{kV}$
m-well	1k ÷ 20k	$\pm 30$		
m <sup>+</sup> diff	20 ÷ 80	$\pm 20$		
m <sup>+</sup> poly	20 ÷ 80			
poly-h	1k ÷ 20k			


key parameters for now

Passive components: res, cap and interconnects

Interconnects

 We have a bench of 5 or 4 metal layers. Some are connected to the silicon



 


M1 is for local connections

M2 is for block connections


M4 is for energy delivery

$L_{tot} = L \times y$


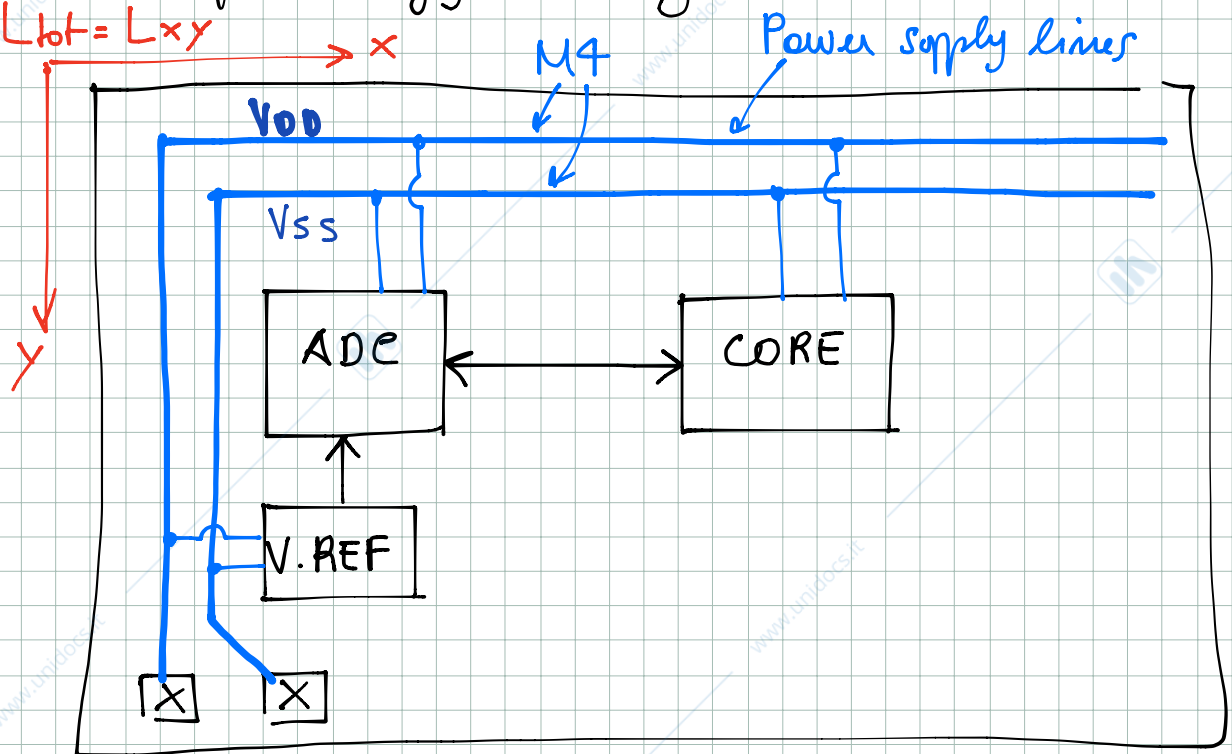


M1	50 ÷ 100	m Ω / □
M2	40 ÷ 80	"
M3	10 ÷ 30	"
M4	3 ÷ 10	"

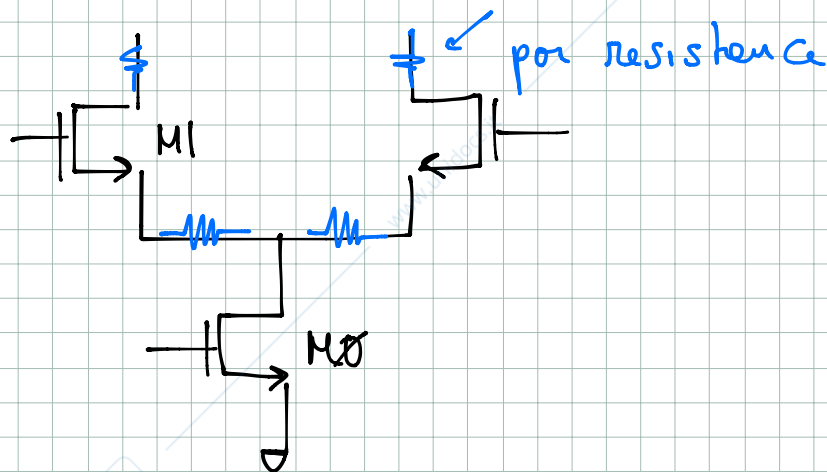
So we increase area going from M1 to M4  
 hence increase res going from M4 to M1.  
 Resistance of interconnection has to be maintained  
 as low as possible (ideally zero).  
 The non-zero resistance of interconnections can  
 interfere with the "nominal" behavior of the circuit




PCB level

 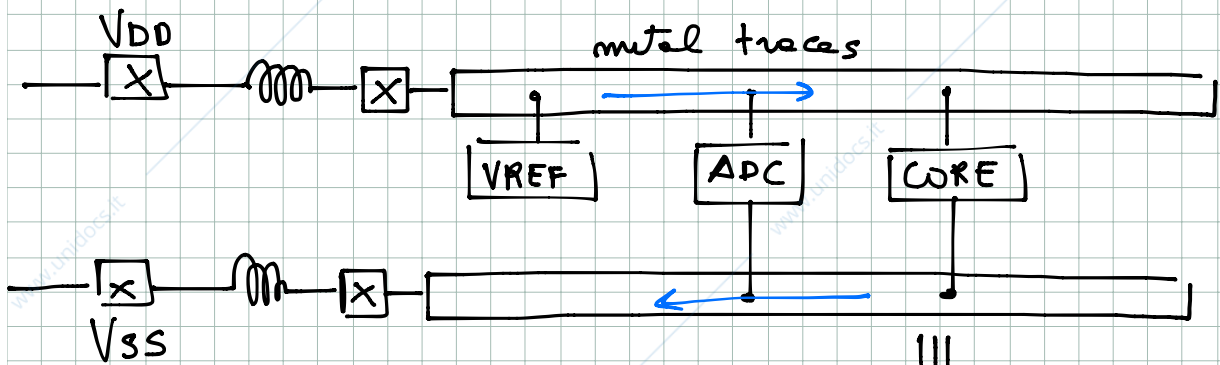

the situation is:

 

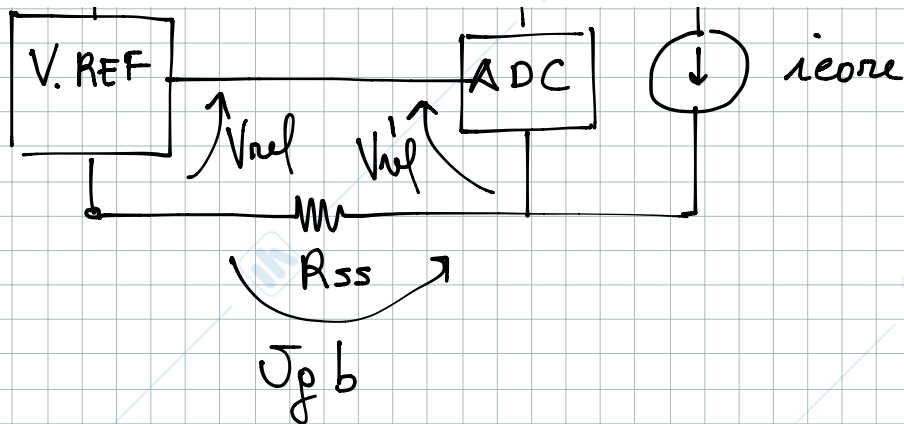

$J_{pb}$  can be comparable with  $V_{ref}$ :

with (M1):  $R_s = 100 \text{ m}\Omega/\square$

$$L \times y = 2 \text{ mm}$$

$$w = 5 \mu\text{m}$$

$$i_{core}, pk = 10 \text{ mA}$$


$$\Rightarrow R_{ss} = 40 \Omega \Rightarrow J_{pb} = 400 \text{ mV}$$


So we have to keep low the impedance of metal interconnections

How about block connections?

Distance like: 2 mm

Effect on current references

 

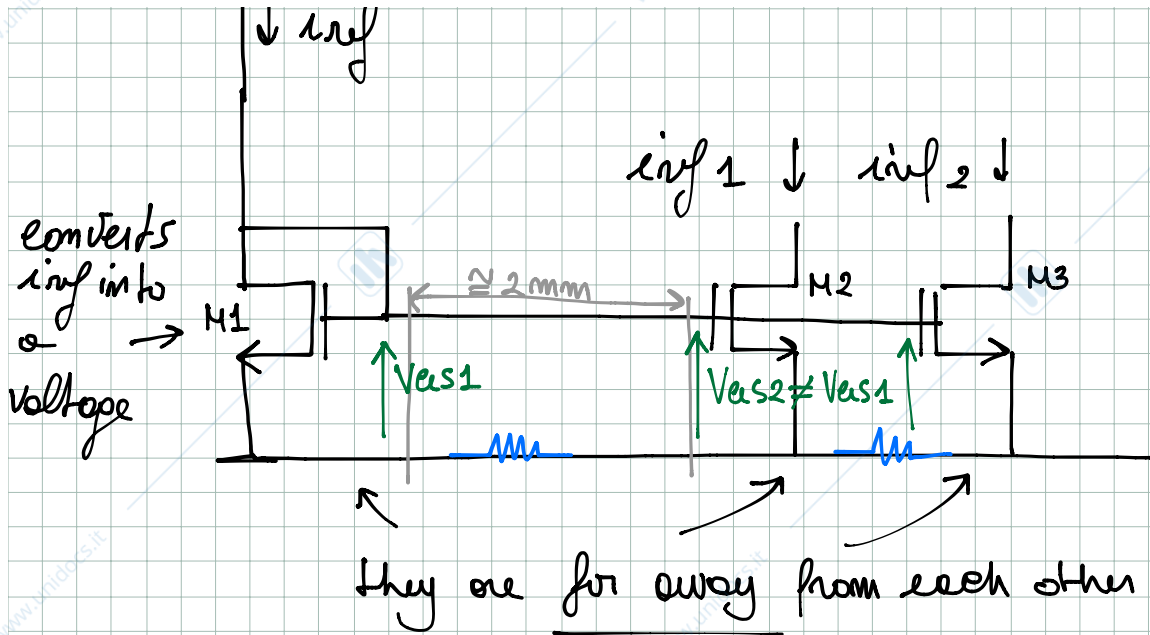


so parasitics resistance of interconnections makes the mirroring factor not to be perfect:


$$\frac{i_{ref1}}{i_{ref}} = \frac{\mu_m \frac{C_{ox}}{2} \left(\frac{W}{L}\right)_2 (V_{GS} - V_{TH})^2}{\mu_m \frac{C_{ox}}{2} \left(\frac{W}{L}\right)_1 (V_{GS2} - V_{TH})^2}$$

we can simplify because tech process is the same

that can't be simplified

The solution is:

 


 

generated by other blocks like the core

Parasitic currents generates a  $\Delta p$  over  $R_{ss}$   
 So this kind of current mirror is not used for far away block but only for very local and close part of the circuit

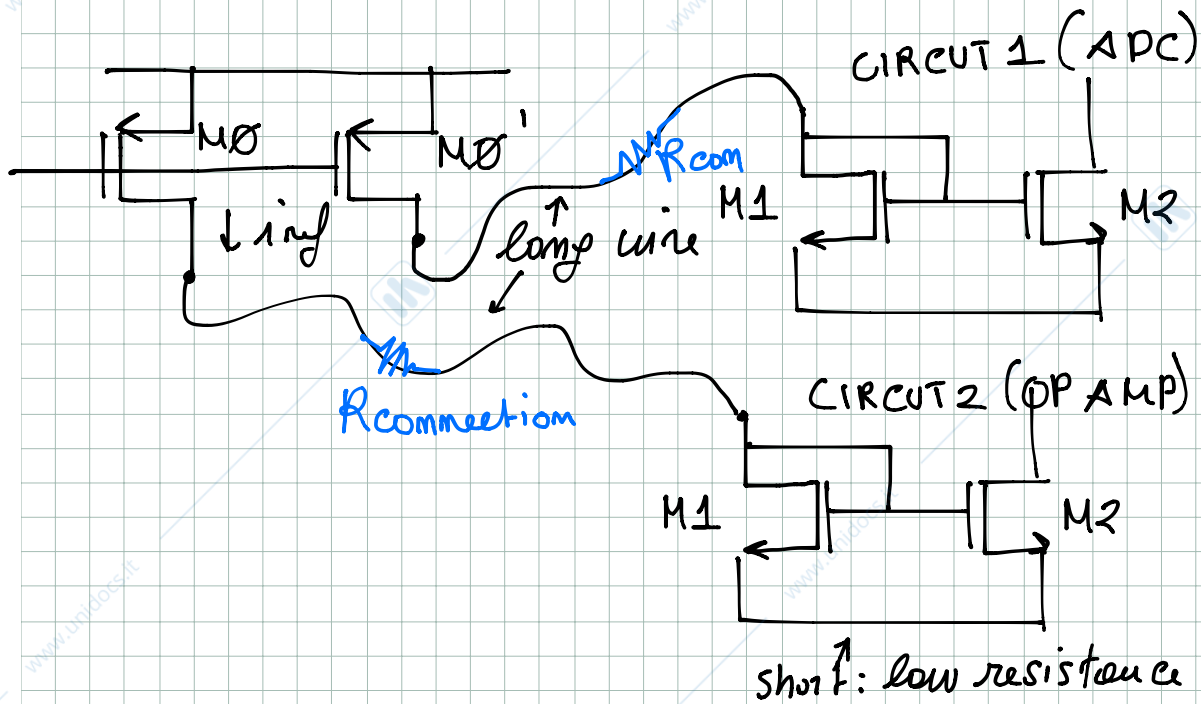
One way to provide inf to other blocks is


 
### "USING" resistance of interconnections

in some cases resistance of interconnections can be exploited to design some part of the circuit, using that resistance like a part of our circuit:  
 for example to measure the current flowing into a block






$$i_{sense} = \frac{V_s}{R_o} = \frac{R_s}{R_o} \cdot i_e$$

to make the sensing circuit to does not consume too much power we have to put

$$R_o \gg R_s \quad \text{like} \quad \frac{R_o}{R_s} = 10^3$$

the ratio between  $R_s$  and  $R_o$  has to be the much constant as possible so they have to be made of the same material and be close one to the other to react the same way at temperature modifications. As  $R_o$  has a big value the sensing circuit does consume a lot of area.

### Capacitors

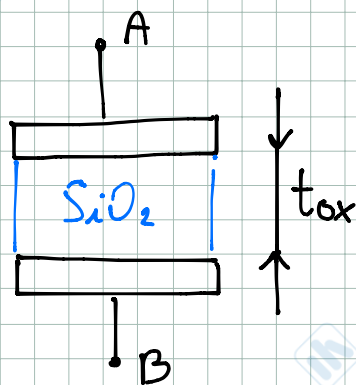


$$C = \epsilon_0 \epsilon_r \frac{W \cdot L}{t_{ox}} = C_{ox} W L$$

### Main parameters for choosing a capacitor


$C_{ox}$

the bigger is that the lower the area is needed to reach a capacitance value.

### MIM Cap

 


### PIP cap

 


$$10^{-2} \frac{fF}{\mu m^2} < C_{ox} < 10^{-1} \frac{fF}{\mu m^2}$$

### Breakdown voltage


### MOS CAP

 

Is thinner but the drawback is:

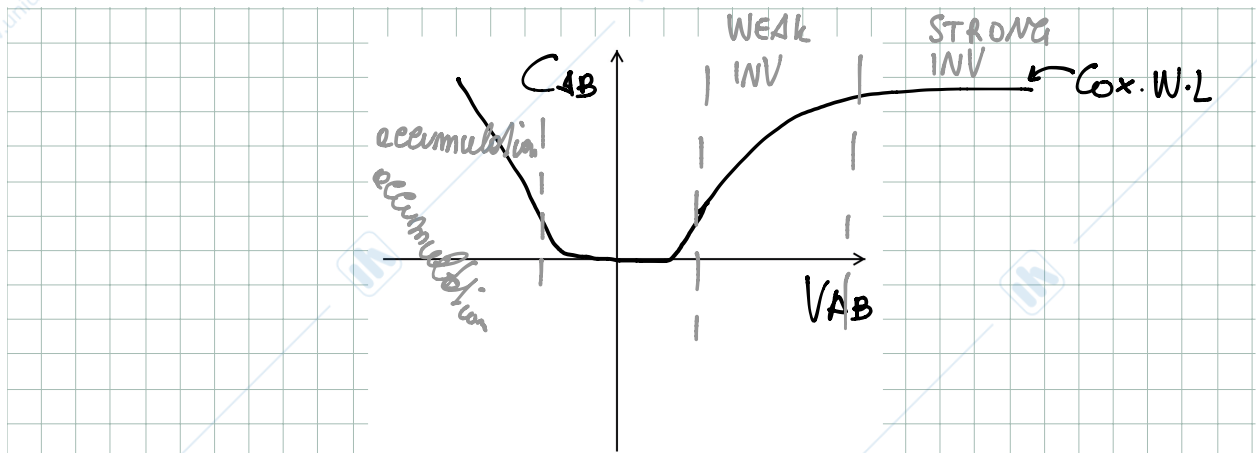

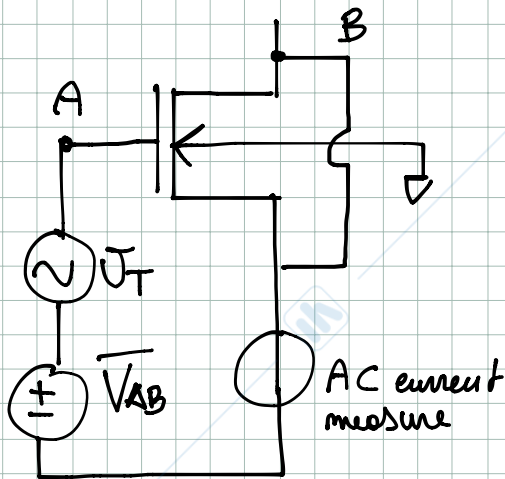Is a non linear capacitor  
Let's examine in detail:




$$C_{ox} \approx 4 \text{ fF}/\mu\text{m}^2$$

$$|Z_{AB}| = \left| \frac{J_g}{i_e} \right| = \frac{1}{\omega C_{AB}}$$

the other kind of capacitor are used to solve bad problems



To solve in part, the non linearity problem we fabricate like this:

 At fab time we put an inversion layer lowering the voltage needed to make the mos work like a cap.





always present lowering  
the voltage needed to reach  
his wanted value

 
 
but it has a drawback: we have parasitics capacitance  $C_j$  so another parameter that classify the cap is  $C_{ox}/C_j$



  these parasitics effects are not positive because the capacitor takes a verse of positioning. For example in a S/H circuit:



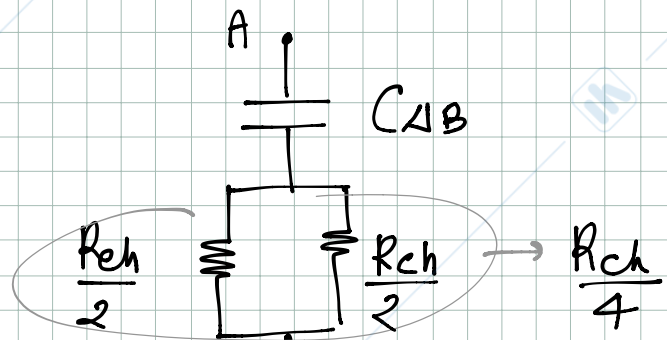 This kind of resistor have parasitics resistances that generates a time of constant for the charge of the resistor generating a bandwidth specification




B

so the time constant is


$$\tau = C_{AB} \cdot \frac{R_{ch}}{4} = \frac{C_{AB}WL}{4} \cdot \frac{1}{\mu_n C_{ox} \frac{W}{L} (V_{AB} - V_{th})^2}$$

$$= \frac{1}{4\mu_n (V_{AB} - V_{th})} L^2$$


mMOS

 


symbols

 


ISO MOS

 


 

symbol

 


isolation effects

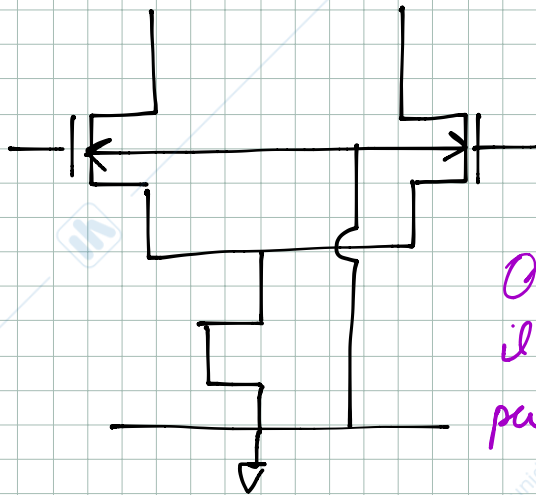

here we have body effect

Qui dobbiamo collegare il body a massa per evitare il latch-up?



with iso

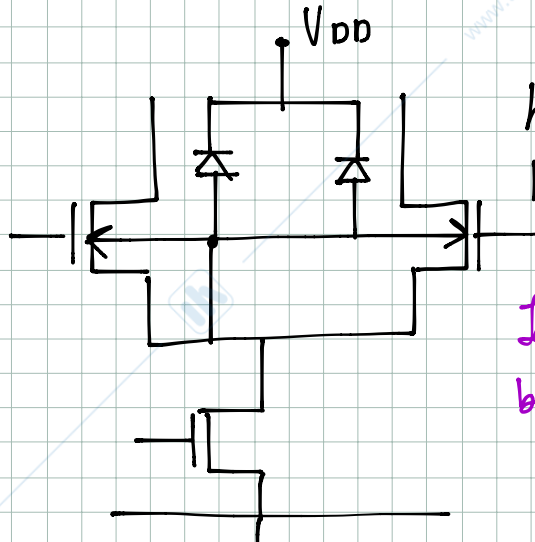


here we don't have body-effect

Invece qui non c'è bisogno

PMOS

  


symbol

 

we can connect it in order to have a not body effect

Fabrication tolerances

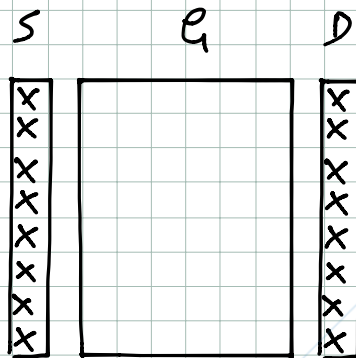

Fabrication tolerances can effect alignments of contacts and shape of contacts making some parameters of the mos varyng

for example, in this expression:


$$I_D = \mu_n \frac{C_{ox}}{L} \left( \frac{W}{L} \right) (V_{GS} - V_{th})^2$$

2 (L)

tolerances affects  $R_{ox}, W, L, V_{th}$ 

but there is an advantage. When two components very close are fabricated at the same time they are affected by the same tolerance errors. This is a very good thing because we can built circuits in order to "cancel the same tolerance".

 For example, if we have two resistor fabricated together



$$R_1 \neq R_{1nominal} \quad R_1 = R_{1m} + \Delta R_1$$

$$R_2 \neq R_{2m} \quad R_2 = R_{2m} + \Delta R_2$$


$$\text{and} \quad \frac{\Delta R_1}{R_{1m}} \approx \frac{\Delta R_2}{R_{2m}}$$

so we can cancel tolerance in this way

$$\frac{R_1}{R_2} = \frac{R_{1m}}{R_{2m}} \frac{\left(1 + \frac{\Delta R_{1m}}{R_1}\right)}{\left(1 + \frac{\Delta R_{2m}}{R_2}\right)}$$


When we have to transfer a voltage to a element we deal with transresistances

|| ; n Vout

 


in the expr  $\frac{V_{ref}}{R_o}$  we have no a ratio of quantities that can equal the toler error. So an unique way to make the

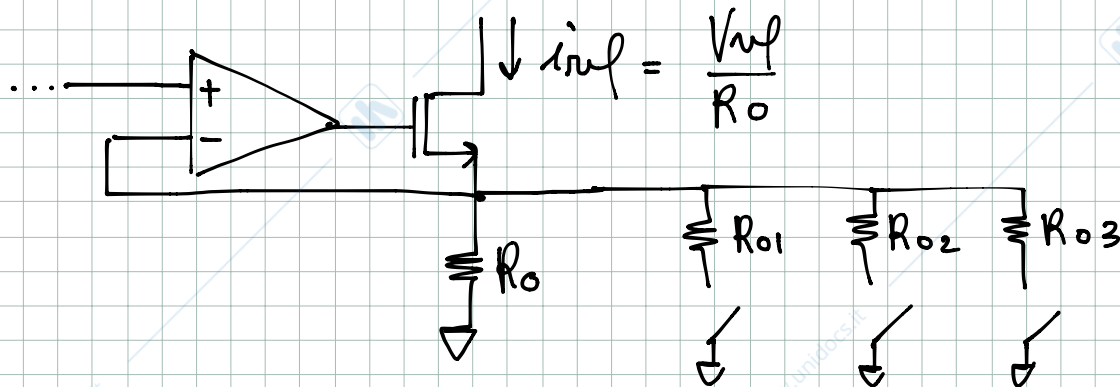circuit work properly is to TRIM every sample that is fabricated. A way to TRIM this circuit is:




we will close or leave opened the switches in order to achieve a resistor value that makes the circuit to work.

Example

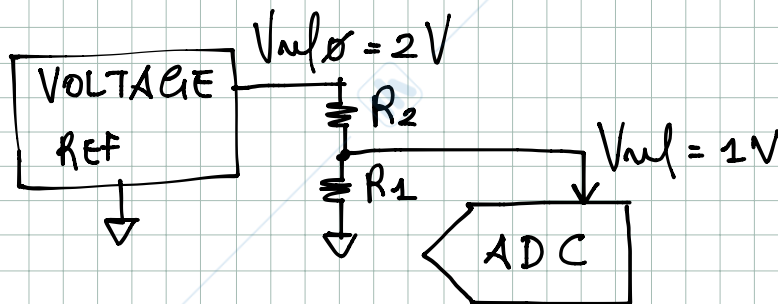


$$\frac{V_{ref1}}{V_{ref2}} = \frac{R_1}{R_1 + R_2} = \frac{1}{1 + \frac{R_2}{R_1}} \leftarrow \text{ratio!}$$

 Sometimes the reference quantity is a current



But if we realize like this:

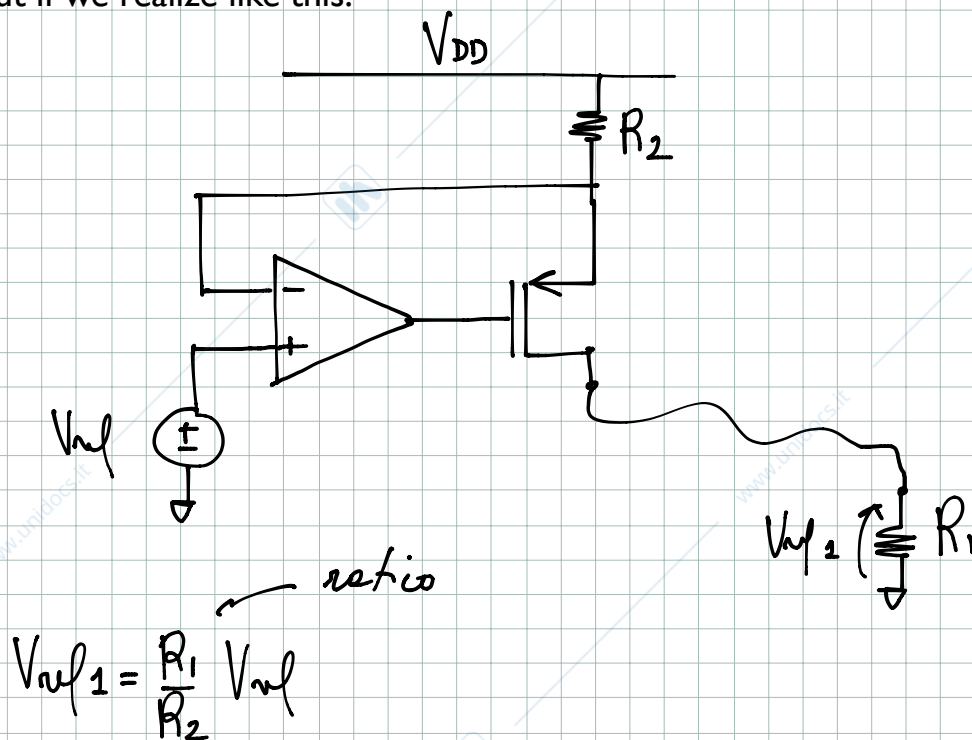

### MISMATCH

We can express mismatch between two resistance with this eq:

$$M = \frac{R_1 - R_2}{R_1 + R_2} \cdot 100\%$$

$$IT = \frac{R_1 + R_2}{2} \cdot I_{CC}$$

Or either with this:

$$\mathcal{J} = \frac{\frac{R_2}{R_1} - \frac{R_{2m}}{R_{1m}}}{\frac{R_{2m}}{R_{1m}}} = \frac{R_{1m}}{R_{2m}} \frac{R_2}{R_1} - 1$$

We will use this eq. because it involves ratio of quantities.

We have a lot of pairs of resistor in the same silicon die, so we can calculate mismatches for everyone:

$$\mathcal{J}_1, \mathcal{J}_2, \dots, \mathcal{J}_N$$


SYSTEMATICAL  
MISMATCH

$$m_{\mathcal{J}} = \frac{1}{N} \sum_{i=1}^N \mathcal{J}_i$$

RANDOM  
MISMATCH

$$S_{\mathcal{J}} = \left[ \frac{1}{N-1} \sum_{i=1}^N (\mathcal{J}_i - m_{\mathcal{J}})^2 \right]^{\frac{1}{2}}$$

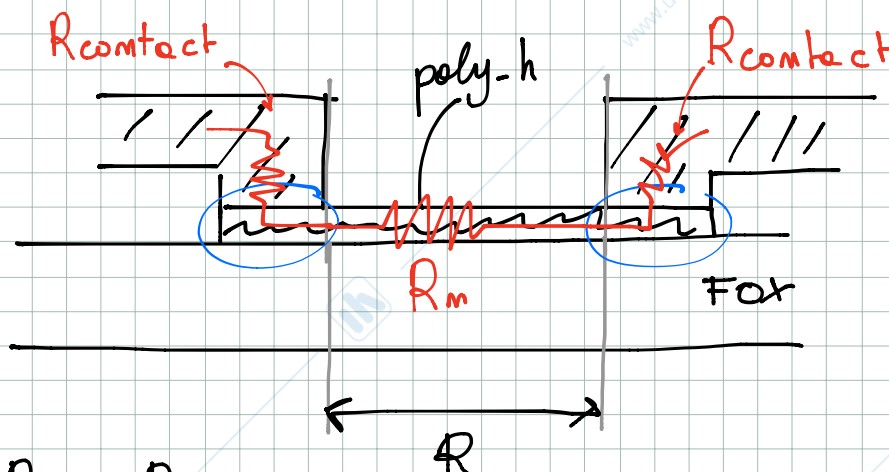Let's apply this eq to a poly\_h resistor:



$$R = R_m + 2R_{\text{contact}}$$


$$\Rightarrow f = \frac{(R_{2m} + 2R_{ctc})}{(R_{1m} + 2R_{ctc})} \cdot \frac{R_{1m}}{R_{2m}} - 1 =$$

$$= \frac{\cancel{R_{2m}} \left(1 + \frac{2R_{ctc}}{\cancel{R_{2m}}}\right)}{\cancel{R_{1m}} \left(1 + \frac{2R_{ctc}}{\cancel{R_{1m}}}\right)} \cdot \frac{\cancel{R_{1m}}}{\cancel{R_{2m}}} - 1 \neq 0$$

$f_{xm}$

$$R_{1m} = 2k\Omega$$


$$R_{2m} = 4k\Omega$$

 


$$R_2 = N R_1 \quad N = 2$$

$$f = \frac{R_2}{R_1} \frac{R_{1m}}{R_{2m}} - 1 = \frac{N R_1}{R_1} \frac{R_{1m}}{N R_{1m}} - 1 = 0$$

 a way to cancel the fab tolerances in presence of  $R_{ctc}$  is to connect in series two resistor in order to make a resistor of the double value, so  $R_2$  could be made in this way:



 

Random mismatches

$S_s$

