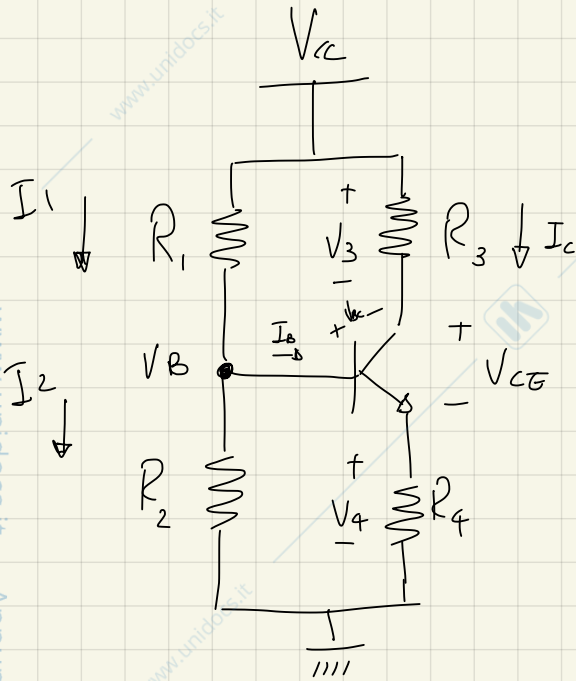


# CIRCUITO AMPLIFICATORE

# Dimensionamento circuito



$$\beta_F = 75$$

$$P = (V_{CE}, I_C) = (6V, 10 \mu A)$$

$$V_{CC} = 18V$$

$$V_3 + V_4 = V_{CC} - V_{CE} = 18 - 6 = 12V$$

$$V_3 = V_4 = \frac{V_3 + V_4}{2} = \frac{12}{2} = 6V$$

$$R_3 = \frac{V_3}{I_C} = \frac{6}{10 \cdot 10^{-6}} = 600 \text{ k}\Omega$$

Assumiamo Regione ATTIVA e Pol. chiusa  $\Rightarrow I_E = I_C + I_B$

$$R_4 = \frac{V_4}{I_E} = \frac{6}{10.77 \cdot 10^{-6}} = 592,11 \text{ k}\Omega$$

Tensione:  $V_{BE} = 0,7V$

$$V_B = V_{BE} + V_4 = 6,7V$$

$$I_B = \frac{I_C}{\beta_F} = \frac{10 \cdot 10^{-6}}{75} = 133,33 \text{ nA}$$

valta  
a caso  
(di Progetto)


$$I_1 = 10 I_B = 1,33 \mu A$$

$$R_1 = \frac{V_{CC} - V_B}{I_1} = \frac{18 - 6,7}{1,33 \cdot 10^{-6}} = 8,34 \text{ k}\Omega$$

$$I_2 = I_1 - I_B = 10 I_B - I_B = 9 I_B$$

$$R_2 = \frac{V_B}{I_2} = \frac{6,7}{9 \cdot 133,33 \cdot 10^{-6}} = 5,56 \text{ k}\Omega$$

Circuito con componenti lineari e

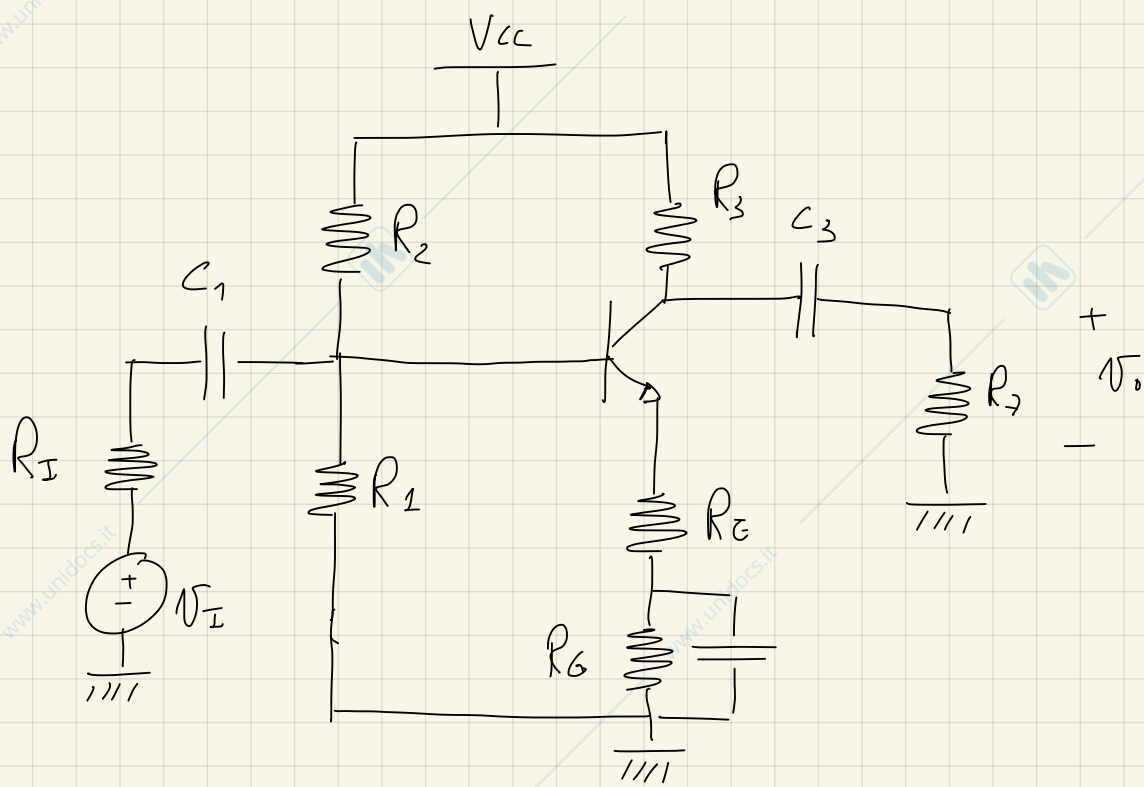


- $V_{CC} = 12V$
- $R_E = 2k$
- $R_1 = 10k$
- $R_2 = 30k$
- $R_3 = 22k$
- $R_E = 3k$
- $R_6 = 10k$
- $R_7 = 100k$


2) Analisi in continua  $f=0 \rightarrow$

$$Z_C = \frac{1}{j\omega C} = \frac{1}{0} = \infty$$

circuito in continua

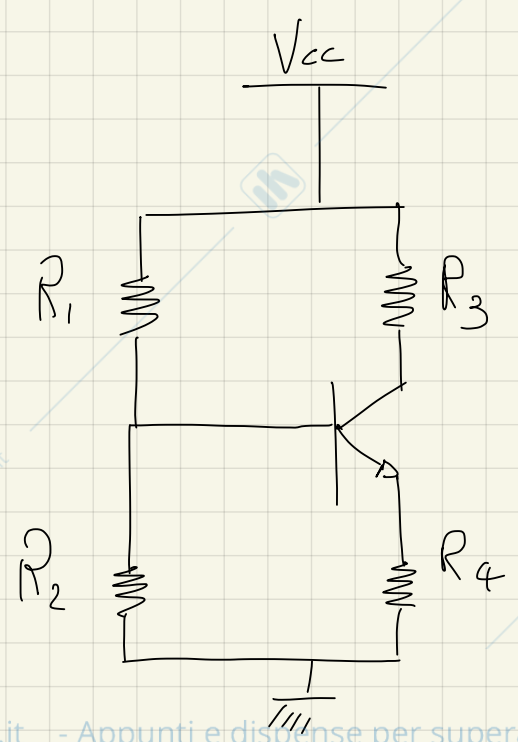

$$R_4 = R_E + R_C = 13k$$

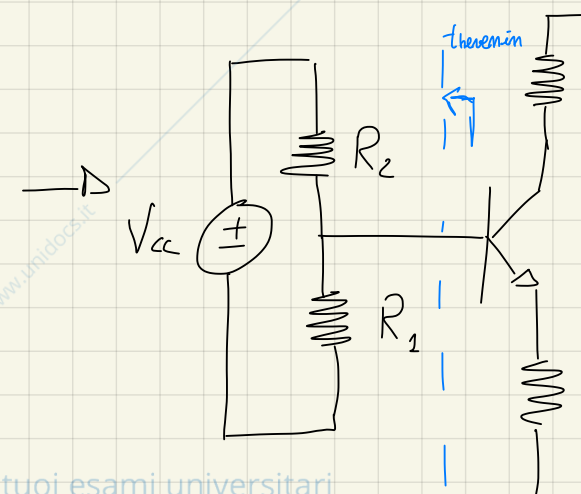

considerazione → Regione ATTIVA

$$I_C = \beta_F \cdot I_B = 100 I_B = 245 \mu A$$

$$V_{BE} = 0,7 V$$

$$I_E = I_B + I_C = 101 I_B = 247,45 \mu A$$

$$\begin{cases} V_{eq} = \dots \\ V_{cc} = \dots \end{cases}$$

$$\begin{cases} V_{eq} = (R_{eq} \dots) \\ V_{cc} = 100 \dots \end{cases}$$

$$I_B = \frac{V_{eq} - V_{BE}}{R_{eq} + 101 R_4} = 2,45 \mu A$$

$$V_{CE} = V_{cc} - (100 R_3 + 101 R_4) I_B = 3,39 V$$


devo controllare che essere dentro

$$V_{BC} = V_B - V_C + V_E = V_{BE} - V_{CE} = -2,69 V < 0$$

$$\underline{P(I_C, V_{CE}) = (245 \mu A, 3,39 V)}$$

analisi in alternata (c → c.c., g)

# BJT Piccoli segnali

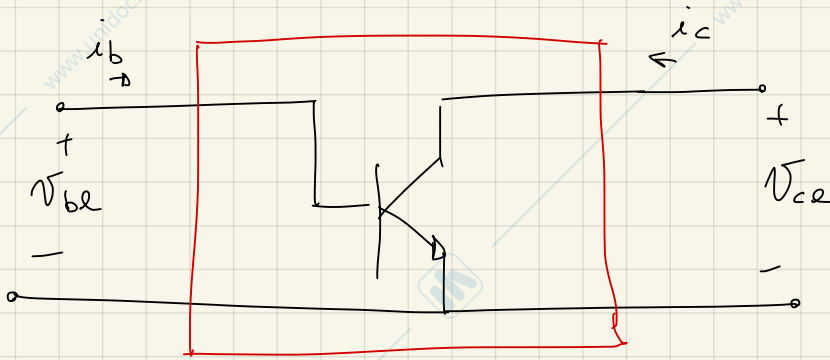

$$\left\{ \begin{aligned} i_c &= \left. \frac{\partial i_c}{\partial v_{be}} \right|_P v_{be} + \left. \frac{\partial i_c}{\partial v_{ce}} \right|_P v_{ce} \\ i_b &= \left. \frac{\partial i_b}{\partial v_{be}} \right|_P v_{be} + \left. \frac{\partial i_b}{\partial v_{ce}} \right|_P v_{ce} \end{aligned} \right.$$

$$i_c = I_S e^{\frac{V_{BE}}{V_T}} \left( 1 + \frac{V_{CE}}{V_A} \right)$$

$$\beta_0 = \frac{\beta_F}{\left( 1 + \frac{V_{CE}}{V_A} \right)}$$

$$i_B = \frac{I_S}{\beta_0} e^{\frac{V_{BE}}{V_T}}$$

$$g_{\pi} = 0$$

$$\beta_0 \approx \beta_F \text{ (remplo)}$$


$$V_T = 25 \text{ mV}$$

$$g_m = \frac{I_S}{V_T} e^{\frac{V_{BE}}{V_T}} \left( 1 + \frac{V_{CE}}{V_A} \right) = \frac{I_C}{V_T} = 9,8 \text{ mS}$$

$$g_o = \frac{I_S}{V_T} e^{\frac{V_{BE}}{V_T}} \frac{1}{V_A + V_{CE}} = \frac{I_C}{V_A + V_{CE}} = 4,59 \mu\text{S}$$

$$g_{\pi} = \frac{g_m}{\beta_F} = 98 \mu\text{S}$$

## Disegno con modello Piccoli segnali

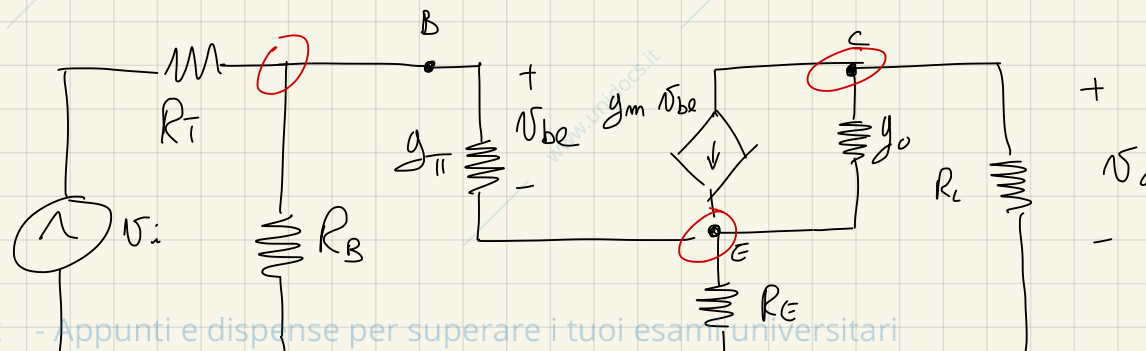


$$\begin{cases} \frac{V_i}{R_I} + g_{\pi} V_e = \left( \frac{1}{R_I} + \frac{1}{R_B} + g_{\pi} \right) V_b \\ (g_m + g_{\pi}) V_b + g_o V_o = \left( \frac{1}{R_E} + g_m + g_{\pi} + g_o \right) V_e = \begin{cases} 5 \cdot 10^{-4} V_i \\ 9,8 \cdot 10^{-3} V_b + 4 \end{cases} \\ (g_m + g_o) V_e = g_m V_b + \left( \frac{1}{R_E} + g_o \right) V_o \end{cases}$$


$$\begin{cases} V_b = -1,92 \cdot 10^{-1} V_o \\ V_e = -1,86 \cdot 10^{-1} V_o \\ V_i = -\frac{V_o}{5,1} \end{cases} \quad A_V = \frac{V_o}{V_i} = -5,1$$
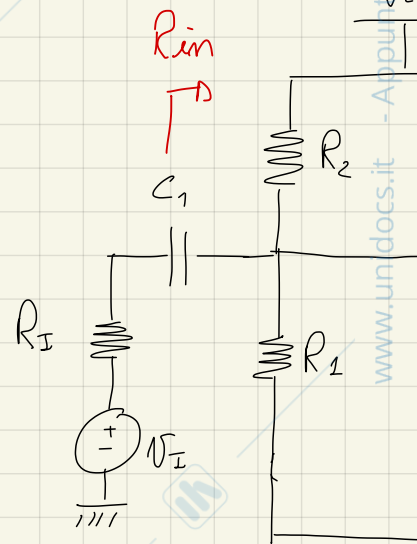
## Resistenza ingresso-unità

Resistenza in genere  
unità da  $C_1$   
in unità da  $C_3$




$R_{in}$

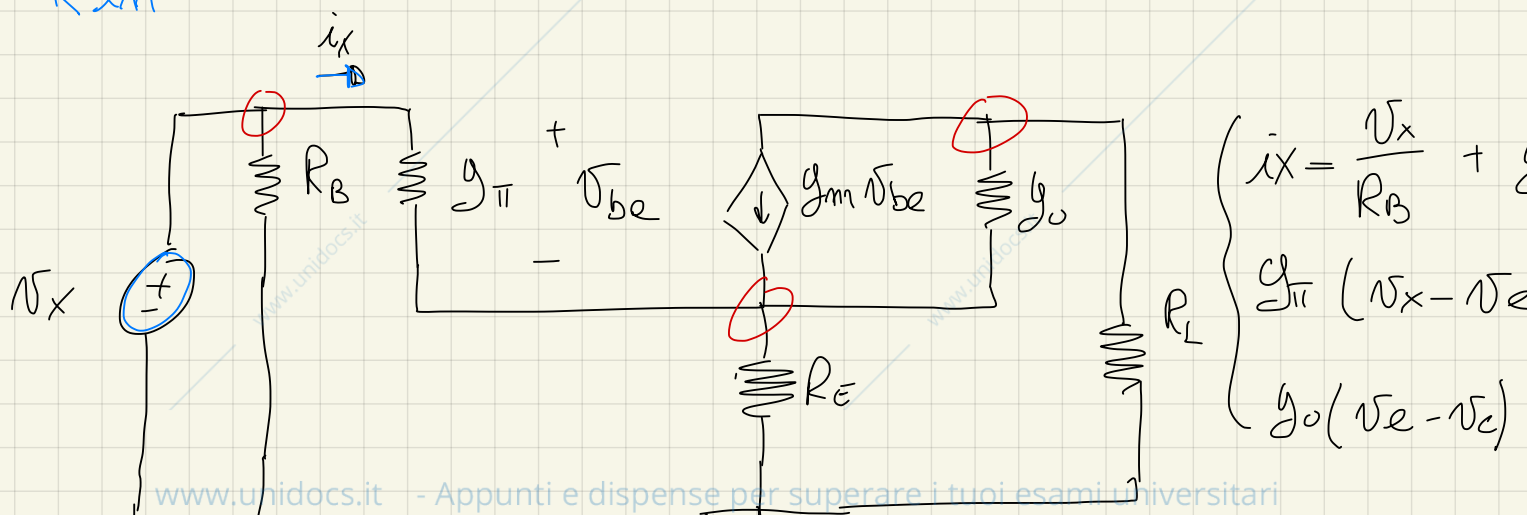


$$\begin{cases} i_x = \frac{v_x}{R_3} + g_o (v_x - v_e) + g_m (v_b - v_e) \\ g_m (v_b - v_e) + g_o (v_x - v_e) = \frac{v_e}{R_e} + g_{\pi} (v_e - v_b) \\ g_{\pi} (v_e - v_b) = \frac{v_b}{R_o} \end{cases}$$

$$R_{out} = \frac{v_x}{i_x} = 21,93 \text{ k}\Omega$$

Dimensionamento

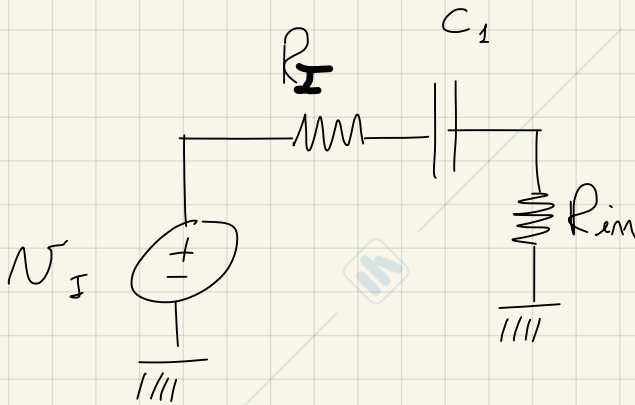


$$R_{eq} = R_I + R_{in}$$

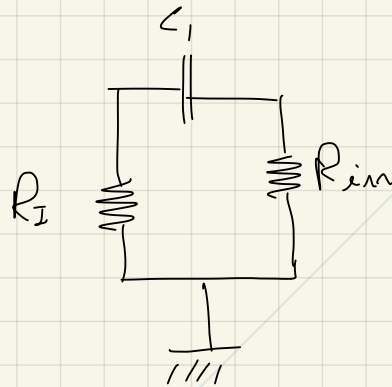

$$\frac{1}{2\pi f_s C_1} \ll R_I + R_{in}$$

$$\frac{100}{2\pi f_s C_1} \ll (R_I + R_{in})$$
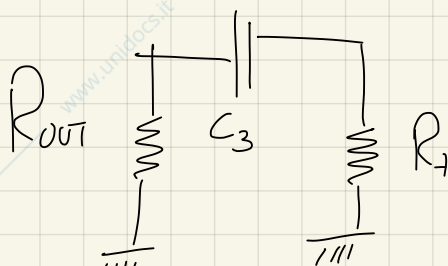
$$C_1 > \frac{100}{2\pi f_s (R_I + R_{in})} = 203 \text{ nF}$$




$$\frac{1}{2\pi f_s C_3} \ll R_7 + R_{out}$$

$$i_x = \frac{V_x}{R_E} + \frac{V_x - V_e}{R_E}$$

$$\frac{V_x - V_e}{R_E} + y_m (V_b - V_e) = g_{\pi} (V_e - V_b) + g_o (V_e - V_c)$$

$$g_{\pi} (V_e - V_b) = \frac{V_b}{R_E}$$

$$R_{ref} = \frac{V_x}{i_x} = 2,3$$

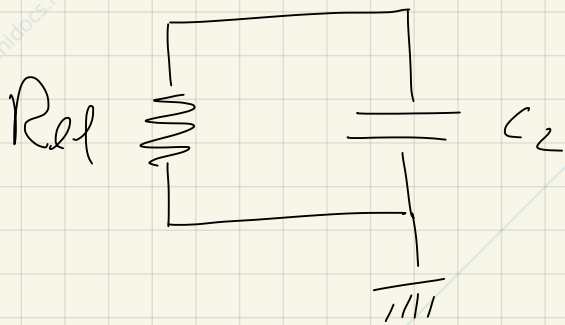

$$\frac{1}{2\pi f_s C_2} \ll R_{ref}$$