



$$\bar{V}_{ab} \longrightarrow \text{e poi } \bar{V}_{ab}(jX_4) \stackrel{?}{=} 0$$

$$\bar{V} = \bar{i}_L \left(\frac{1}{j\omega C_3} + j\omega L_3 + R_1 \right) = \bar{i}_R (R_1 + jX_4) = \bar{V}_s$$

$$\bar{i}_L R_1 = \bar{i}_R jX_4 \quad (\bar{V}_{ab} \equiv 0)$$

$$\left\{ \begin{array}{l} \bar{V}_s = (R_1 + jX_4) \bar{i}_R \\ \bar{V}_s = \left(\frac{1}{j\omega C_3} + j\omega L_3 + R_1 \right) \bar{i}_L \\ \bar{i}_L = \bar{i}_R j \frac{X_4}{R_1} \end{array} \right.$$

$$\frac{(R_1 + jX_4) \cancel{\bar{i}_R}}{} = 1$$

$$\left(\frac{1}{j\omega C_3} + j\omega L_3 + R_1 \right) j \frac{X_4}{R_1} \cancel{\bar{i}_R}$$

$$R_1 + jX_4 = j \frac{X_4}{R_1} \left(\frac{1}{j\omega C_3} + j\omega L_3 + R_1 \right)$$

$$R_1 + jX_4 = j \frac{X_4}{R_1} \left(\frac{1}{j\omega C_3} + j\omega L_3 + R_1 \right)$$

$$R_1 + jX_4 = \frac{X_4}{R_1 \omega C_3} + \frac{\omega L_3 X_4}{R_1} + j \frac{X_4}{R_1}$$

$$R_1 = X_4 \left(\frac{1}{R_1 \omega C_3} - \frac{\omega L_3}{R_1} \right)$$

$$\omega \neq \sqrt{\frac{1}{L_3 C_3}}$$

$$X_4 = R_1 \frac{\omega R_1 C_3}{1 - \omega^2 L_3 C_3} = \frac{\omega R_1^2 C_3}{1 - \omega^2 L_3 C_3}$$

$$T = 2000 \quad \omega = \frac{2\pi}{2000}$$

$$X_4 = \frac{\pi}{1000} \cdot \frac{10^4 \cdot 4.7 \cdot 10^{-6}}{1 - \left(\frac{\pi}{1000}\right)^2 \cdot 0.098 \cdot 4.7 \cdot 10^{-6}} =$$

$$= \frac{\pi}{1000} \cdot \frac{4.7 \cdot 10^{-2}}{1 - \frac{\pi^2}{10^6} \cdot 10^{-6} \cdot 4.7 \cdot 0.098} = -41.641 \mu\Omega$$

=

