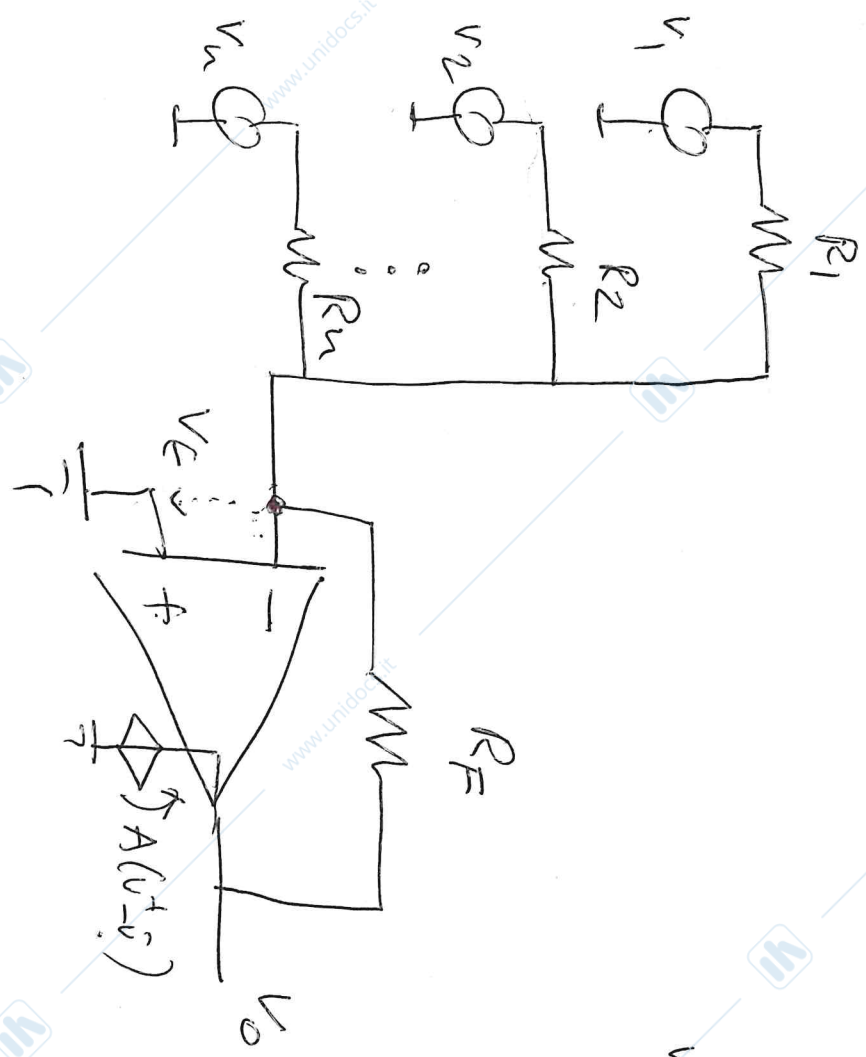



AMPLIFICATORE SOMMATORE



$$G_{ID} = \frac{v_0/v_2}{v_2} = -\frac{R_F}{R_2}$$


$$\Rightarrow v_0/v_2 = -v_2 \frac{R_F}{R_2}$$

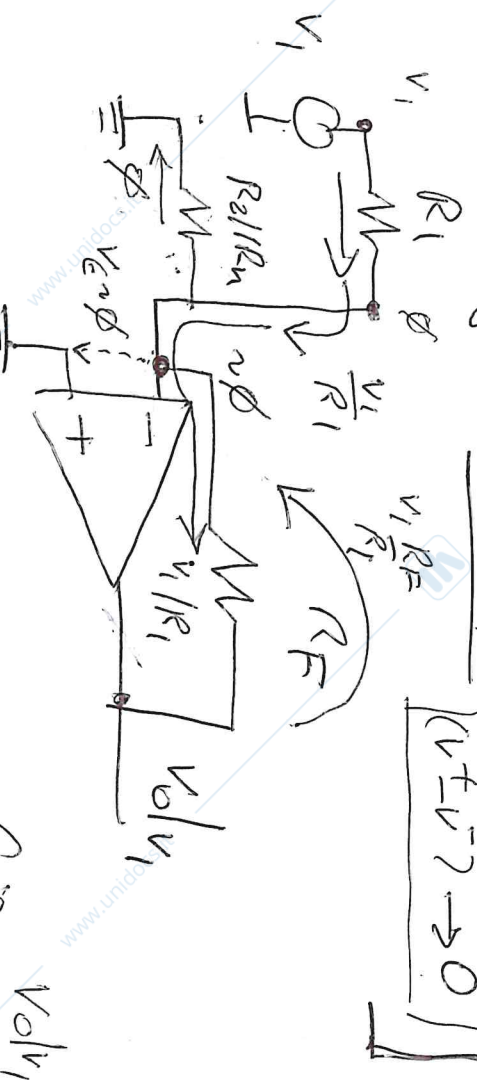Cualquier ideal $(A \rightarrow \infty)$
 $(v^- \rightarrow 0)$




$$\Rightarrow v_0/v_1 = -v_1 \frac{R_F}{R_1}$$
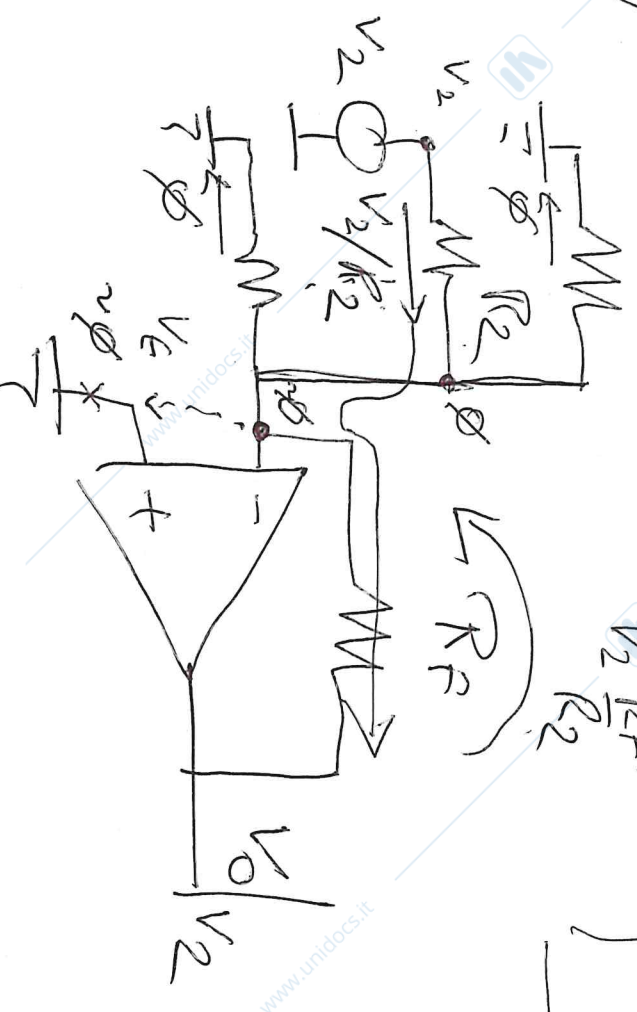
$$G_{ID} = \frac{v_0/v_1}{v_1} = -\frac{R_F}{R_1}$$



$$v_0/v_2$$

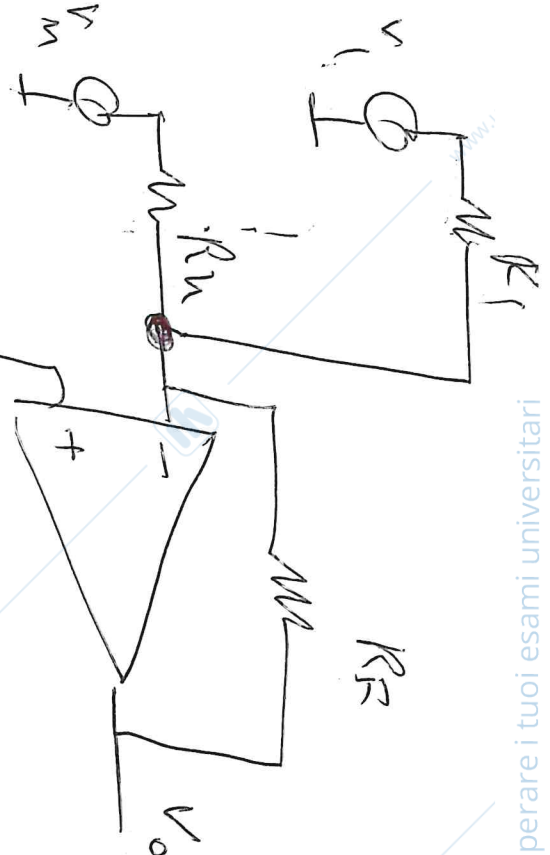

$$Y_{R} = G_{id} \left[\frac{-G_L}{1 - G_L} \right]$$

GUADAGNO D'ANELLO (G_{loop}) - v_{gate} x v_{in} e FLT


SEMPRE POSITIVO DEI TRANSISTORI

$$v_o = - \left[v_1 \frac{R_F}{R_1} + v_2 \frac{R_F}{R_2} + \dots + v_n \frac{R_F}{R_n} \right]$$

CASO PARTICOLARE R₁ = R₂ = ... = R_n = R_L

$$v_o = - \frac{R_F}{R_L} (v_1 + v_2 + \dots + v_n)$$

$$R_{eq} = R_1 || R_2 || \dots || R_n$$

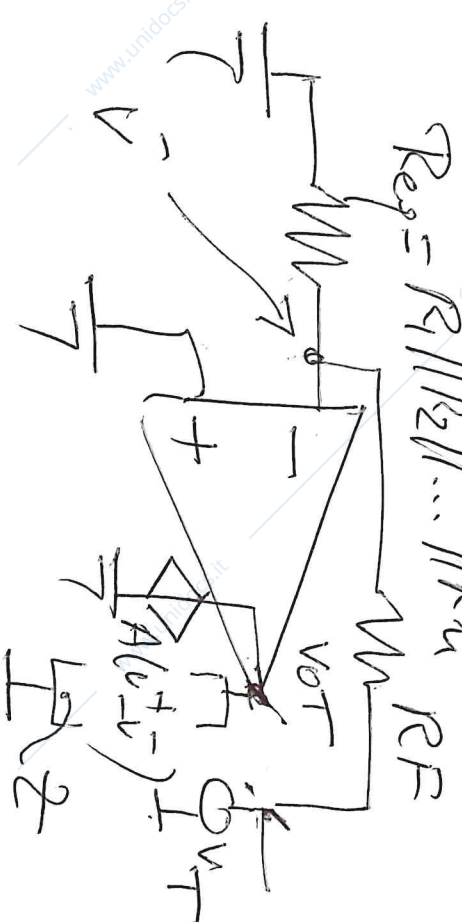


$$v = v_T \frac{R_{eq}}{R_{eq} + R_F}$$


$$v_{OT} = -A \frac{R_{eq}}{R_{eq} + R_F} v_T$$

$$\Rightarrow G_{loop} = \frac{v_{OT}}{v_T} = -A \frac{R_{eq}}{R_{eq} + R_F}$$


#1) MIXER AUDIO/VIDEO

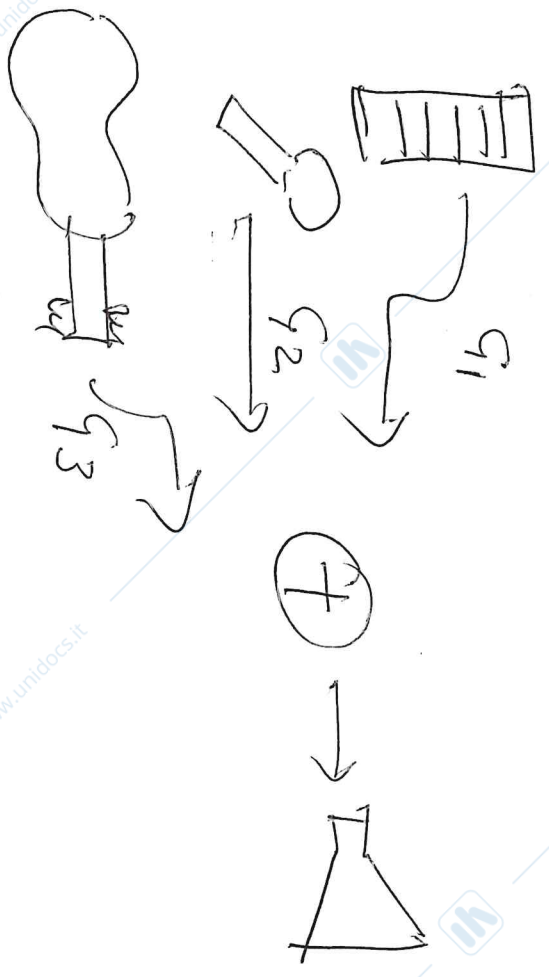

#2) AC + DC

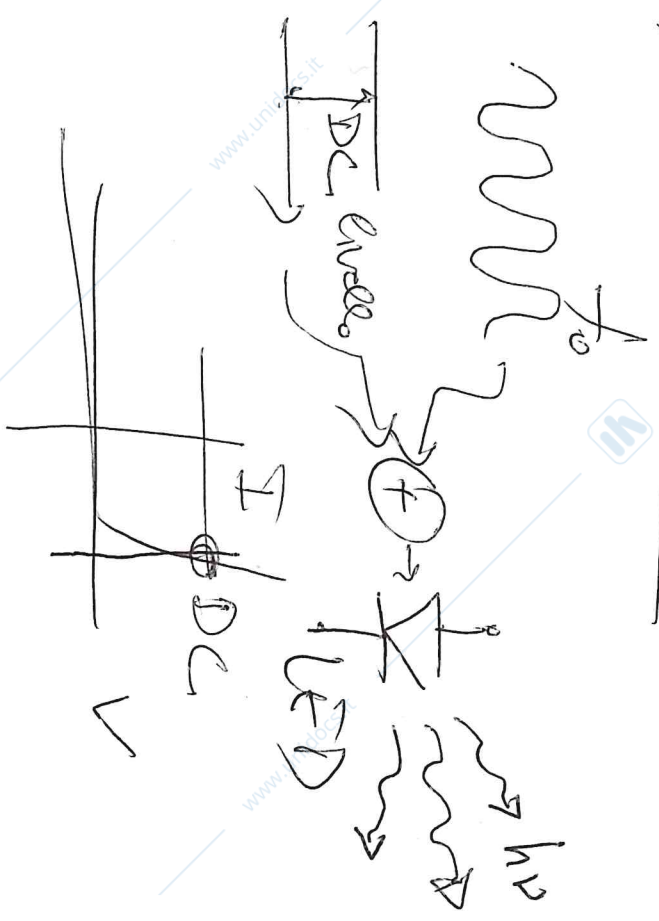


13) D/A CONVERTER

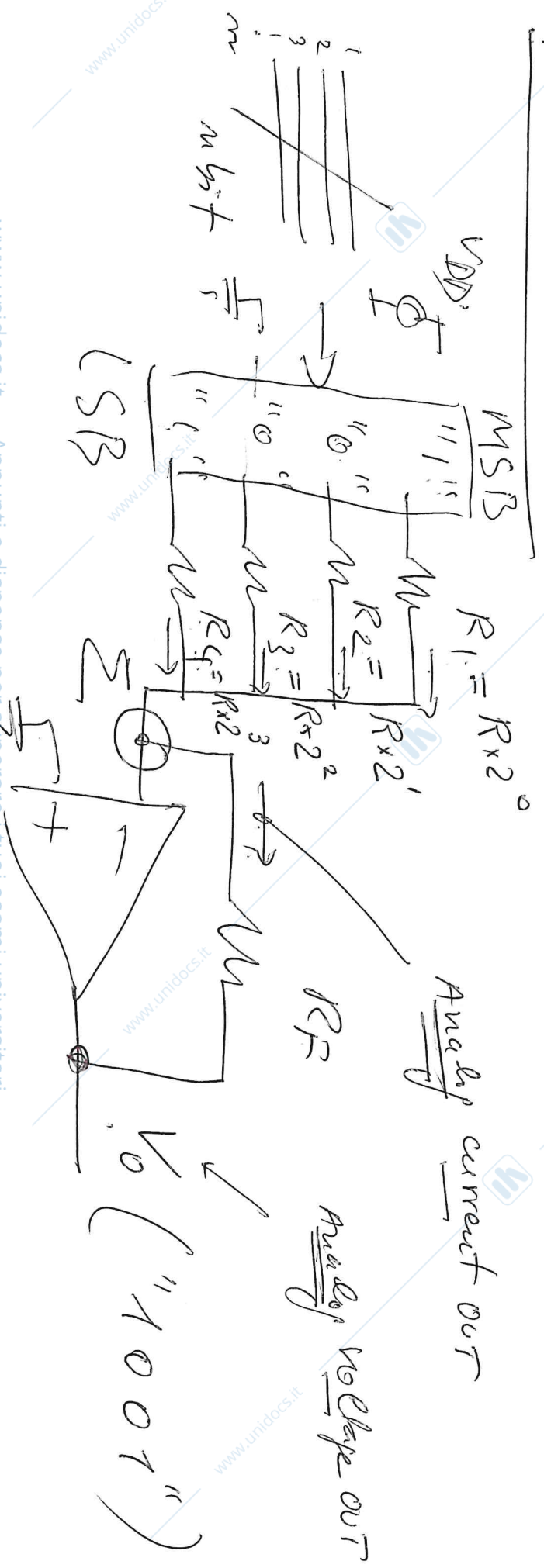

AMPLIFICATORE SOSTRATTIVO

(DEVE DIFFERENZIALE)

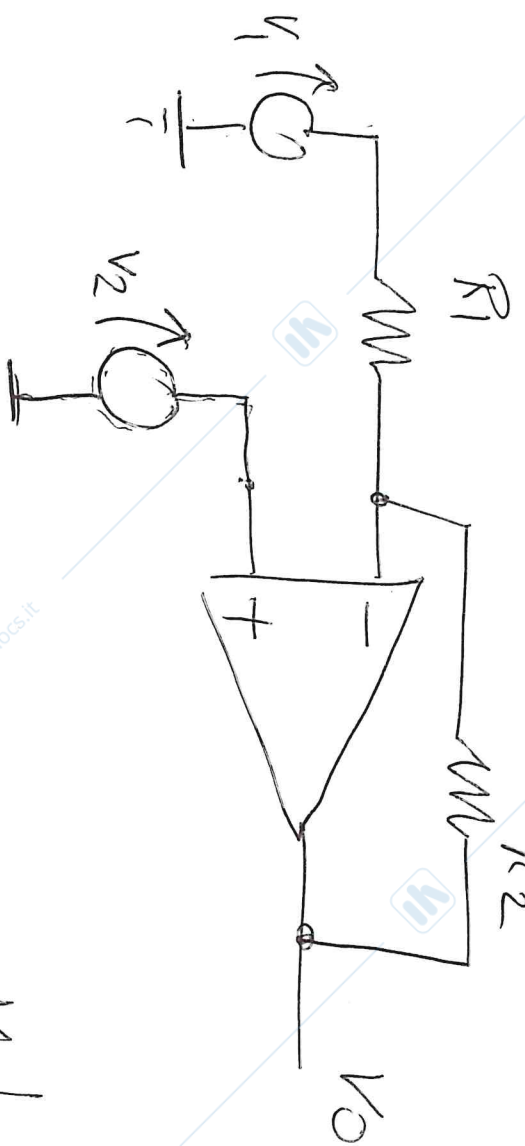


$$V_0/V_1 = \left(-\frac{R_2}{R_1} \right) \cdot V_1$$

$$V_0/V_2 = \left(1 + \frac{R_2}{R_1} \right) \cdot V_2$$

$$\rightarrow V_0 = V_0/V_1 + V_0/V_2 = \left(-\frac{R_2}{R_1} \right) V_1 + \left(1 + \frac{R_2}{R_1} \right) V_2$$

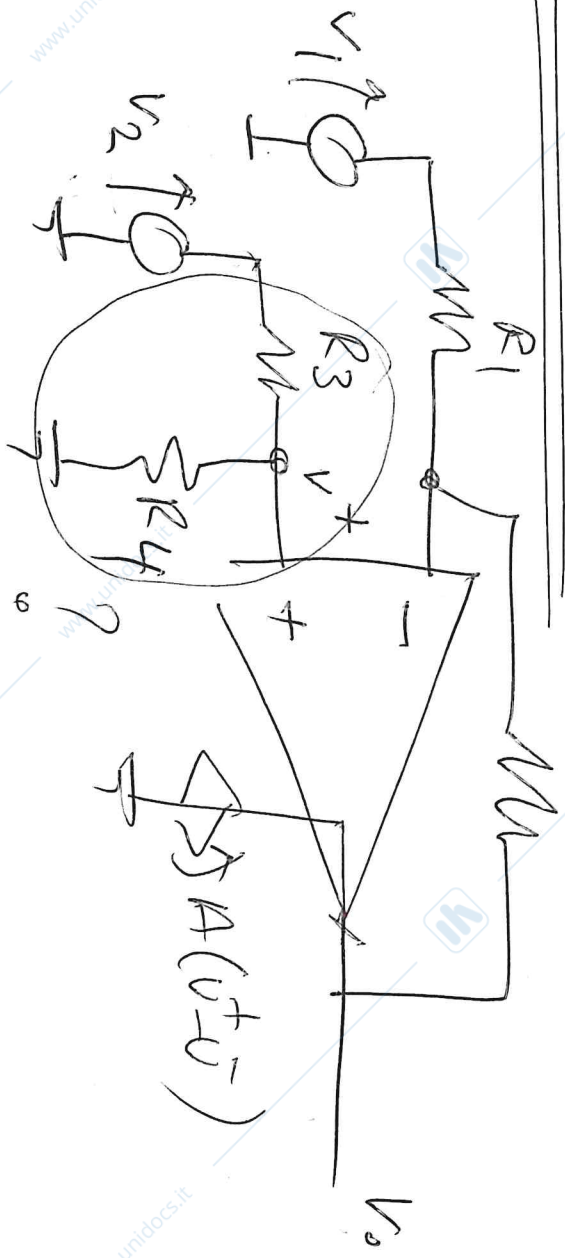
$$V_0 \stackrel{?}{=} (V_1 - V_2) \cdot R_2$$



Sovra posizione e l'elce (GND)


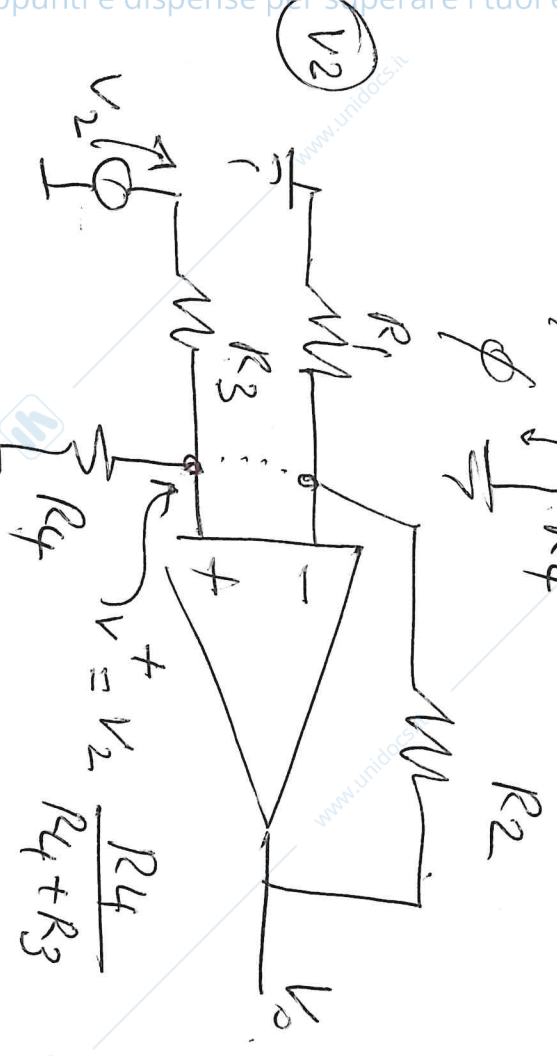
$$\rightarrow V_0/V_1 = \left(-\frac{R_2}{R_1}\right) \cdot V_1 \left(\frac{\text{coef.}}{1 \text{ inv.}}\right)$$



$$\rightarrow V_0/V_2 = \underbrace{V_2 \left(\frac{R_4}{R_4+R_3}\right)}_{V^+} \cdot \underbrace{\left(1 + \frac{R_2}{R_1}\right)}_{V^+}$$

(coef. non inv.)

$$V_1 + V_2 \Rightarrow V_0 = -\left[\frac{R_2}{R_1}\right] \cdot V_1 + \underbrace{\left[\frac{R_4}{R_3+R_4} \cdot \left(1 + \frac{R_2}{R_1}\right)\right]}_{G_2} \cdot V_2 = \underbrace{-G_1}_{G_1} V_1 + \underbrace{G_2}_{G_2} V_2$$

Se $\frac{R_2}{R_1} = \frac{R_4}{R_3+R_4} \rightarrow G_1 = G_2 = G \Rightarrow \boxed{V_0 = G(V_2 - V_1)}$

$$\frac{R_2}{R_1} = \frac{R_4/R_3}{R_2/R_3} \left(1 + \frac{R_2}{R_1}\right)$$


↑
valore R_2/R_1

↑
valore R_4/R_3

CONDIZIONE PER AVERE
 $V_0 = G(V_2 - V_1)$

$$\begin{cases} k_1 = \frac{R_2}{R_1} \\ k_2 = \frac{R_4}{R_3} \end{cases} \Rightarrow k_1 = \frac{k_2}{1 + k_2} (1 + k_1)$$
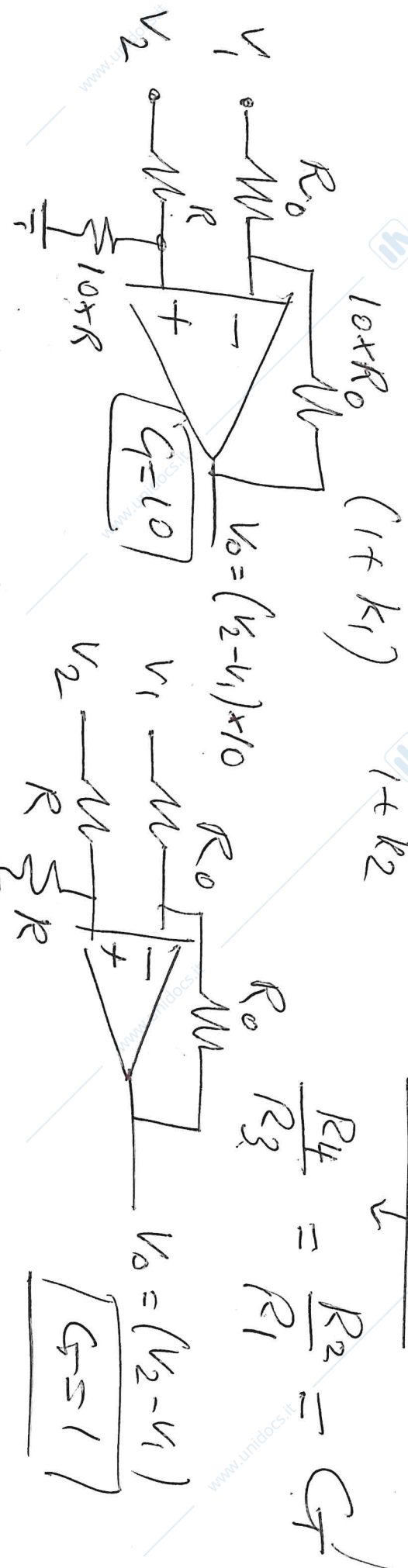
$$\frac{k_1}{(1 + k_1)} = \frac{k_2}{1 + k_2} \Rightarrow k_1 = k_2$$



CANCELLAZIONE DISTURBI E.M. CON LETTORA DIFFERENZIALE (4)

