

Contents

- [esercizio asincrono](#)
- [Calcolo parametri](#)
- [caratteristica linearizzata](#)
- [calcolo scorrimento nominale](#)
- [dati generatore sincrono](#)
- [ese trafo parallelo](#)

esercizio asincrono

```
clear all
```

```
Pn=10e3
```

```
Vn=380
```

```
rendn=0.9
```

```
Rs=0.45
```

```
cosfin=0.89
```

```
n=3
```

```
pcc=10/100
```

```
vcc=15/100
```

```
po=20/100
```

```
Io=15
```

```
Tl=20
```

Pn =

10000

Vn =

380

rendn =

0.9000

Rs =

0.4500

cosfin =

0.8900

n =

3

pcc =

0.1000

vcc =

0.1500

po =

0.2000

Io =

15

Tl =

20

Calcolo parametri

$$P_{cc} = p_{cc} \cdot P_n$$

$$V_{cc} = v_{cc} \cdot V_n$$

$$P_o = p_o \cdot P_n$$

$$P_{fe} = P_o - 3 \cdot R_s \cdot I_o^2$$

$$I_n = (P_{fe} + P_n + P_{cc}) / (\sqrt{3} \cdot V_n \cdot \cos \phi_{in})$$

$$R_o = V_n^2 / P_{fe}$$

$$\cos \phi_{io} = P_{fe} / (\sqrt{3} \cdot V_n \cdot I_o)$$

$$X_o = V_n^2 / (P_{fe} \cdot \tan(\arccos(\cos \phi_{io})))$$

$$R_r = (P_{cc} - 3 \cdot R_s \cdot I_n^2) / (3 \cdot I_n^2)$$

$$\cos \phi_{ic} = P_{cc} / (\sqrt{3} \cdot V_{cc} \cdot I_n)$$

$$X_d = (P_{cc} \cdot \tan(\arccos(\cos \phi_{ic}))) / (3 \cdot I_n^2)$$

Pcc =

1000

Vcc =

57

Po =

2000

Pfe =

1.6963e+03

In =

21.6741

Ro =

85.1290

cosfio =

0.1718

Xo =

14.8470

Rr =

0.2596

cosfic =

0.4673

Xd =

1.3424

caratteristica linearizzata

```

om=2*pi*50
k=n*Vn^2/(om*Rr)
x=Tl/k
omega_m=om/n*(1-x)
Ir=(Vn/sqrt(3))/(sqrt((Rs+Rr/x)^2+Xd^2))
Pass=3*(Rs+Rr/x)*Ir^2+Pfe
Qass=3*Xd*Ir^2+(Pfe*tan(acos(cosfio)))
Is=sqrt(Pass^2+Qass^2)/(sqrt(3)*Vn)
rend=(Tl*omega_m)/(Pass)

```

om =

314.1593

k =

5.3123e+03

17/2/2016

appello040216

x =

0.0038

omega_m =

104.3255

Ir =

3.1609

Pass =

3.7763e+03

Qass =

9.7661e+03

Is =

15.9087

rend =

0.5525

calcolo scorrimento nominale

$$A = (P_n * (R_s^2 + X_d^2) + R_r * V_n^2)$$

$$B = 2 * R_s * R_r * P_n - V_n^2 * R_r$$

$$C = P_n * R_r^2$$

$$x_n = (-B + \sqrt{B^2 - 4 * A * C}) / (2 * A)$$

$$x_{2n} = (-B - \sqrt{B^2 - 4 * A * C}) / (2 * A)$$

A =

5.7526e+04

B =

-3.5146e+04

C =

673.7746

v_n =

x11 =

0.5911

x2n =

0.0198

dati generatore sincrono

```

Ans=20e3
Vns=380
cosfins=0.8
xs=150/100
Veccn=20
Ieccn=3
rendns=0.9
Pl=10e3
cosfil=0.78
Ins=Ans/(sqrt(3)*Vns)
Xs=xs*Vn/(sqrt(3)*Ins)
Pcus=(Ans*cosfins*(1-rendns)-rendns*(Veccn*Ieccn))/rendns

Rss=Pcus/(3*Ins^2)

Il=Pl/(sqrt(3)*Vn*cosfil)
Er=Vn/sqrt(3)+Rss*Il*cosfil+Xs*Il*sin(acos(cosfil))
Ei=-Rss*Il*sin(acos(cosfil))+Xs*Il*cosfil
E=sqrt(Er^2+Ei^2)

Ern=Vn/sqrt(3)+Rss*Ins*cosfins+Xs*Ins*sin(acos(cosfins))
Ein=-Rss*Ins*sin(acos(cosfins))+Xs*Ins*cosfins
En=sqrt(Ern^2+Ein^2)
Vecc=E*Veccn/En
delta=atan(Ei/Er)
Recc=Veccn/Ieccn
rendns=Pl/(Pl+3*Rss*Il^2+Vecc^2/Recc)

```

Ans =

20000

Vns =

380

cosfins =

0.8000

xs =

1.5000

Veccn =

20

Ieccn =

3

rendns =

0.9000

P1 =

10000

cosfil =

0.7800

Ins =

30.3869

Xs =

10.8300

Pcus =

1.7178e+03

Rss =

0.6201

Il =

19.4788

Er =

360.8261

Ei =

156.9860



E =

393.4972

Ern =

431.9216

Ein =

251.9657

En =

500.0430

Vecc =

15.7385

delta =

0.4104

Recc =

6.6667

rends =

0.9308

ese trafo parallelo

```

I2t=100
cosfi2t=0.8
V1nt=1500
Anat=40e3
vccat=4/100
Anbt=20e3
vccb=5/100
cosfict=0.6
K=5
V20=V1nt/K
Vccat=vccat*V20
Vccb=vccb*V20
I2nat=Anat/V20
I2nbt=Anbt/V20
Pccat=Vccat*I2nat*cosfict
Pccb=Vccb*I2nbt*cosfict

Rccat=Pccat/I2nat^2

```

```

Rccbt=Pccbt/I2nbt^2
Xccat=Rccat*tan(acos(cosfi2t))
Xccb= Rccbt*tan(acos(cosfi2t))
Zat=Rccat+j*Xccat
Zbt=Rccb+j*Xccb
Zpar=Zat*Zbt/(Zat+Zbt)
Rpar=real(Zpar)
Xpar=imag(Zpar)
deltaV=(Rpar*I2t*cosfi2t+Xpar*I2t*sin(acos(cosfi2t)))
V2t=V20-deltaV
I2at=I2t*Zbt/(Zat+Zbt)
I2bt=I2t*Zat/(Zat+Zbt)
alfa1=abs(I2at)/I2nat
alfa2=abs(I2bt)/I2nbt

rend
rendtot=(V2t*I2t*cosfi2t)/(V2t*I2t*cosfi2t+Rpar*I2t^2)

```

I2t =

100

cosfi2t =

0.8000

V1nt =

1500

Anat =

40000

vccat =

0.0400

Anbt =

20000

vccb =

0.0500

cosfi2t =

0.6000

K =

5

$V_{20} =$

300

$V_{ccat} =$

12

$V_{ccbtt} =$

15

$I_{2nat} =$

133.3333

$I_{2nbt} =$

66.6667

$P_{ccat} =$

960

$P_{ccbtt} =$

600

$R_{ccat} =$

0.0540

$R_{ccbtt} =$

0.1350

$X_{ccat} =$

0.0720

$X_{ccbtt} =$

0.1800

$Z_{at} =$

$$0.0540 + 0.0720i$$

$$Z_{bt} =$$

$$0.1350 + 0.1800i$$

$$Z_{par} =$$

$$0.0386 + 0.0514i$$

$$R_{par} =$$

$$0.0386$$

$$X_{par} =$$

$$0.0514$$

$$\text{delta}V =$$

$$6.1714$$

$$V_{2t} =$$

$$293.8286$$

$$I_{2at} =$$

$$71.4286$$

$$I_{2bt} =$$

$$28.5714 - 0.0000i$$

$$\text{alfa}1 =$$

$$0.5357$$

$$\text{alfa}2 =$$

$$0.4286$$

$$\text{rend} =$$

$$0.5525$$

$$\text{rendtot} =$$

$$0.9839$$



Published with MATLAB® R2015a

www.unidocs.it - Appunti e dispense per superare i tuoi esami universitari

www.unidocs.it - Appunti e dispense per superare i tuoi esami universitari

www.unidocs.it

www.unidocs.it

www.unidocs.it

www.unidocs.it

www.unidocs.it

www.unidocs.it

