

$W = ?$   
 $A = ?$   
 $I_1', I_2', I_3' = ?$

CARICO B

$P_B = 3 R_B I_B^2 \rightarrow$

$I_B = \sqrt{\frac{P_B}{3 R_B}} = 5 A$

$E_B = \sqrt{R_B^2 + X_B^2} I_B = 224 V$

$\frac{Q_B}{P_B} = \tan \phi_B$

$\phi_B = 27^\circ = \tan^{-1} \frac{X_B}{R_B}$

Quindi

$\tan^{-1} \frac{X_B}{R_B} = \tan^{-1} \frac{Q_B}{P_B} \rightarrow X_B = R_B \frac{Q_B}{P_B} = 20 \Omega$

In alternativa:

$P_B = 3 E_B I_B \cos \phi_B \rightarrow E_B = \frac{3000}{3 \cdot 5 \cdot \cos 27^\circ} = 224 V$

Alle rete  $S_1$ :

$$P_{S1} = P_B + P_A = 5000 \text{ W}$$

$$Q_{S1} = Q_B + Q_A \quad \text{con:}$$

$$A_A = \sqrt{P_A^2 + Q_A^2} \rightarrow |Q_A| = \sqrt{A_A^2 - P_A^2} = 917 \text{ VAR}$$

per cui dall'indicazione "out of phase"  $\bar{e}$ :

$$Q_A = -917 \text{ VAR}$$

Quindi:

$$S_1 \left\{ \begin{array}{l} P_{S1} = 5000 \text{ W} \\ Q_{S1} = 1500 - 917 = 583 \text{ VAR} \\ E_{S1} = E_B = 224 \text{ V} \end{array} \right. \rightarrow I_{S1} = \frac{\sqrt{P_{S1}^2 + Q_{S1}^2}}{3E_{S1}} = 7.5 \text{ A}$$

Alle rete  $S_2$ :

$$S_2 \left\{ \begin{array}{l} P_{S2} = P_{S1} + 3 \cdot R_C \cdot I_{S1}^2 = 5844 \text{ W} \\ Q_{S2} = Q_{S1} = 583 \text{ VAR} \\ I_{S2} = I_{S1} = 7.5 \text{ A} \end{array} \right. \rightarrow E_{S2} = \frac{\sqrt{P_{S2}^2 + Q_{S2}^2}}{3I_{S2}} = 261 \text{ V}$$


posto  $\bar{E}_1$  a fase nulla in lue:

$$\bar{E}_1 = 261 e^{j0} \rightarrow \bar{V}_{12} = 261 e^{j30^\circ}; \bar{V}_{23} = 261 e^{-j90^\circ}$$

$$\bar{I}_1 = 7.5 e^{-j6^\circ}$$

nota: la fase  $\bar{e}$  è stata calcolata osservando che  $Q_{S2} > 0$  (corrente in ritardo) e che  $\varphi_{S2} = \arctan \frac{Q_{S2}}{P_{S2}} = 6^\circ$
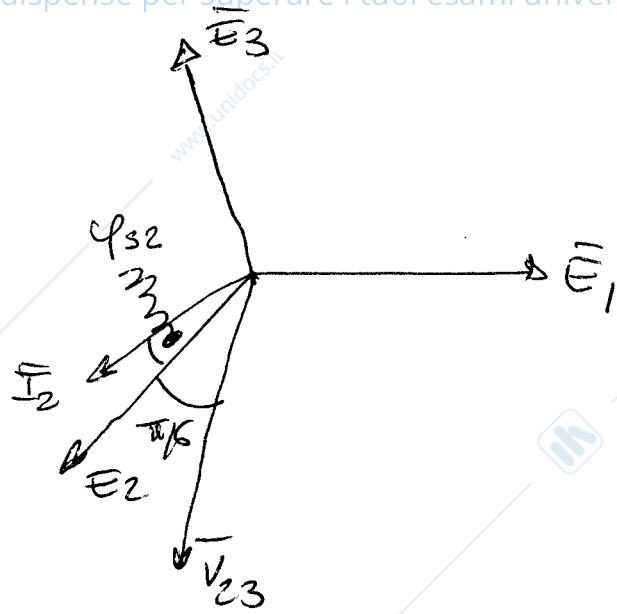
$$\begin{aligned}
 W &= \bar{V}_{23} \cdot \bar{I}_2 = \\
 &= \sqrt{3} E_{S2} I_{S2} \cos(30^\circ + 6^\circ) = \\
 &= 2743 \text{ W}
 \end{aligned}$$



Riguardo il carico equilibrato, si ha:

$$\bar{V}_{20'} = 0$$

$$\bar{I}_L = \frac{\bar{V}_{10'}}{jX_{LD}} = \frac{\bar{V}_{12}}{jX_{LD}} = \frac{261 e^{j30^\circ}}{j70} = 1.86 - j 3.23$$

$$\bar{I}_C = \frac{\bar{V}_{30'}}{-jX_{CD}} = \frac{\bar{V}_{32}}{-jX_{CD}} = \frac{-261 e^{-j90^\circ}}{-j70} = -3.73$$

Infine:

$$\text{lettore amperometro} \rightarrow |\bar{I}_L + \bar{I}_C| = 3.73 \text{ A}$$

$$\bar{I}'_1 = \bar{I}_1 + \bar{I}_L = 9.32 - j 4.01$$

$$\bar{I}'_2 = \bar{I}_2 - (\bar{I}_L + \bar{I}_C) = 2.54 - j 2.84$$

$$\bar{I}'_3 = \bar{I}_3 + \bar{I}_C = -6.78 + j 6.85$$

